

Electrical Training

Week 2: Common Circuit Elements, Series vs. Parallel, KVL & KCL, Circuits on Breadboards

Agenda



- Resistors, Capacitors, Inductors, Diodes/LEDs, FETs
- Circuit Analysis
 - Nodes & Junctions
 - Series vs. Parallel
 - KVL & KCL
- Measurements
- Circuits & Breadboards

Resistors






- Element that inhibits the flow of electrons
- Changes flow of current



Capacitors



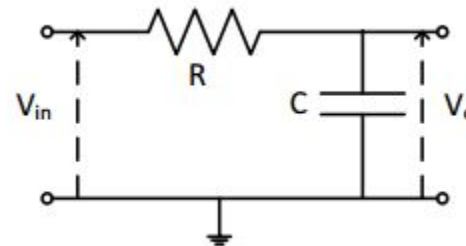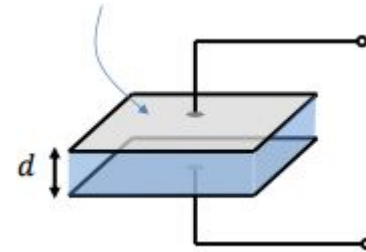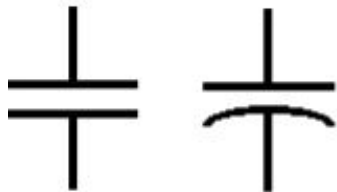
- Element that temporarily stores electrical energy
 - polarized
 - non-polarized



What is an Inductor?



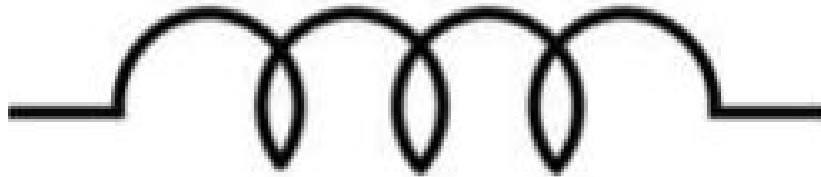
- Element that temporarily stores energy in the form of a magnetic field among its coils





Diodes and LEDs



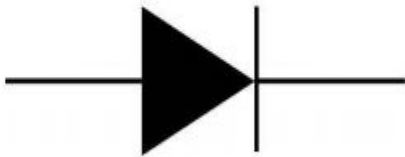- Element that limits the flow of electrons to one direction
- Forward Bias: $V_+ > V_-$
- Reverse Bias: $V_- > V_+$
- Unbiased: $V_+ == V_-$
-





colored plastic lens

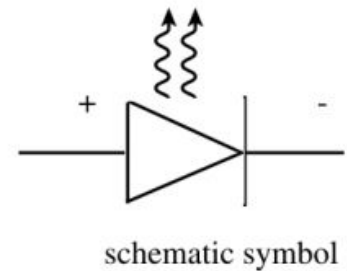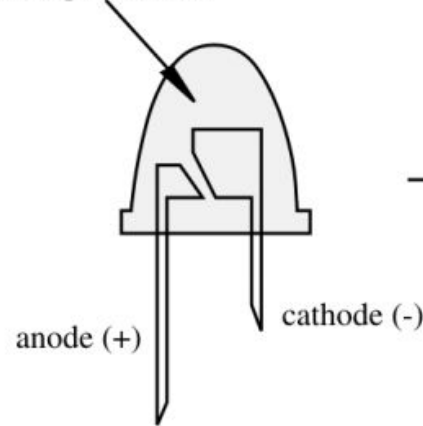

Field Effect Transistors (FET)



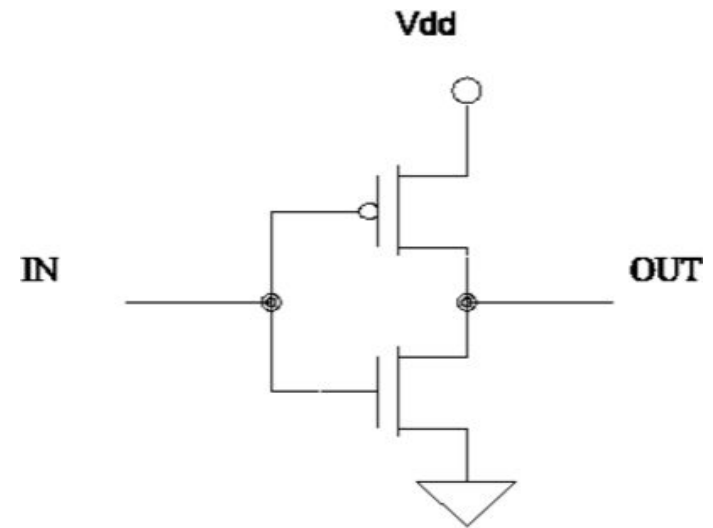
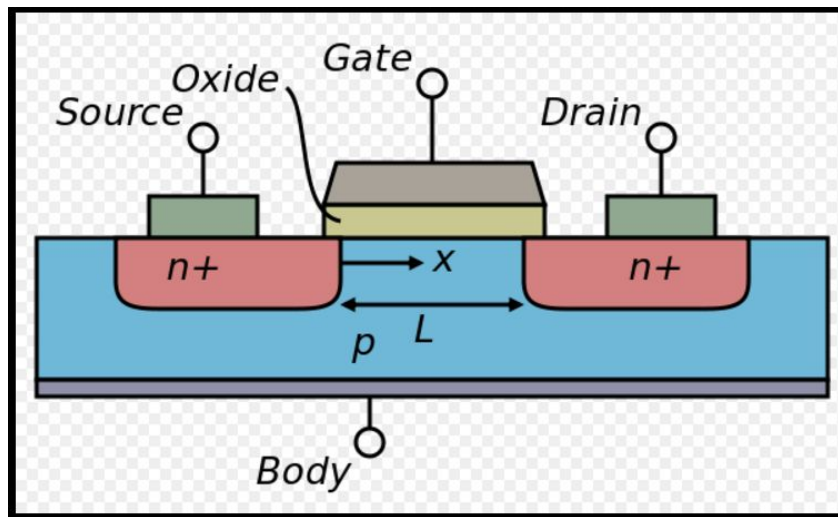
- Field Effect Transistors - Controls electric conductivity of a channel



Operational Amplifiers (OP Amps)




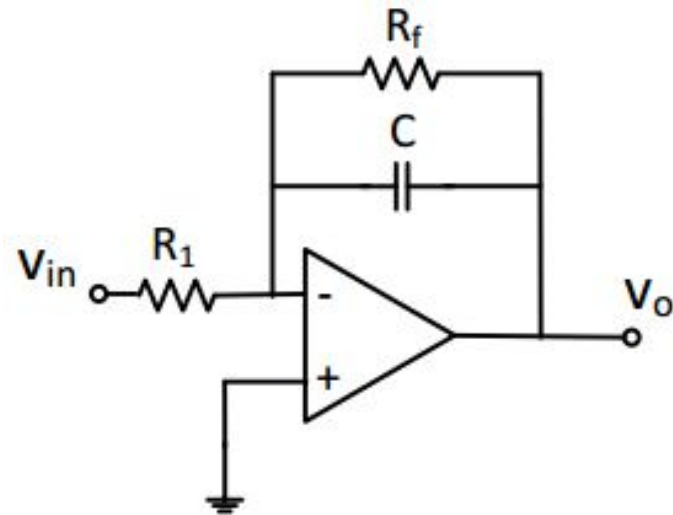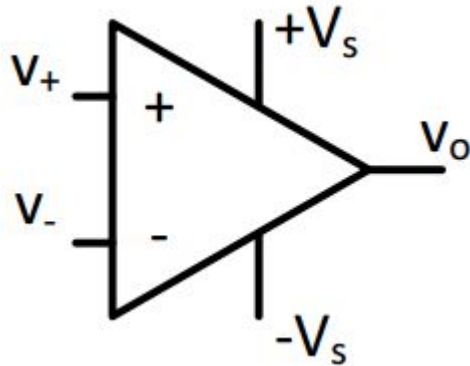- Op amps are active devices that can be used to filter or amplify signals.
- Boosts power without changing waveform.




Summary of RC and RLC (Passive) Filters


RC Lowpass:

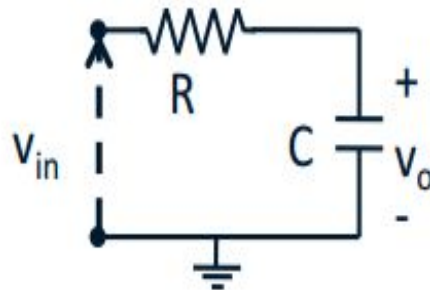




RC Highpass:

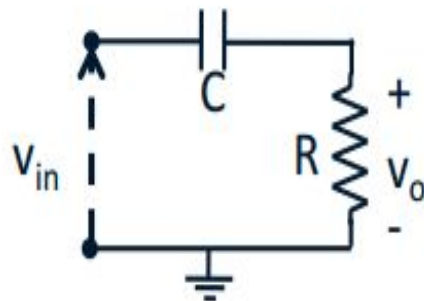

RLC Lowpass:

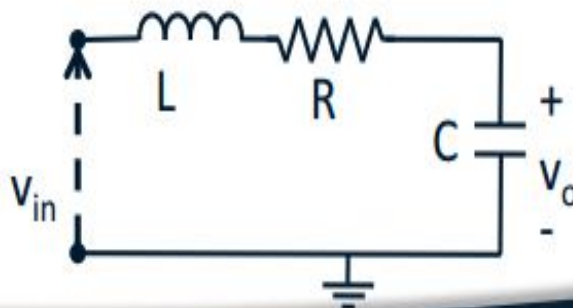

Bode Plots

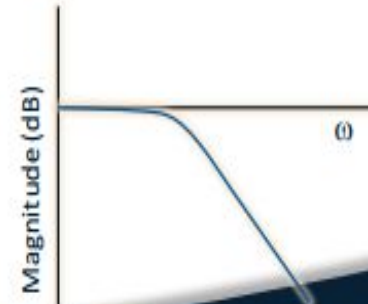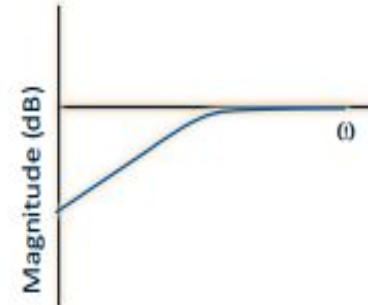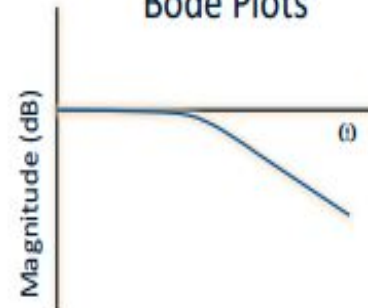





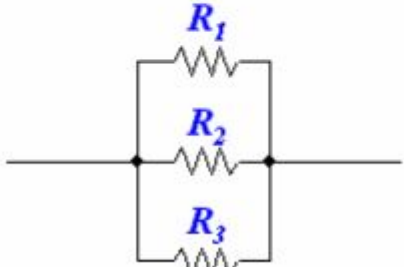

Circuit Analysis



Series vs. Parallel

- Series → Same Current (I)
- Parallel → Same Voltage (V)


Series:  =  $R_{eq} = R_1 + R_2 + R_3$

Parallel:  =  $R_{eq} = (1/R_1 + 1/R_2 + 1/R_3)^{-1}$

Node



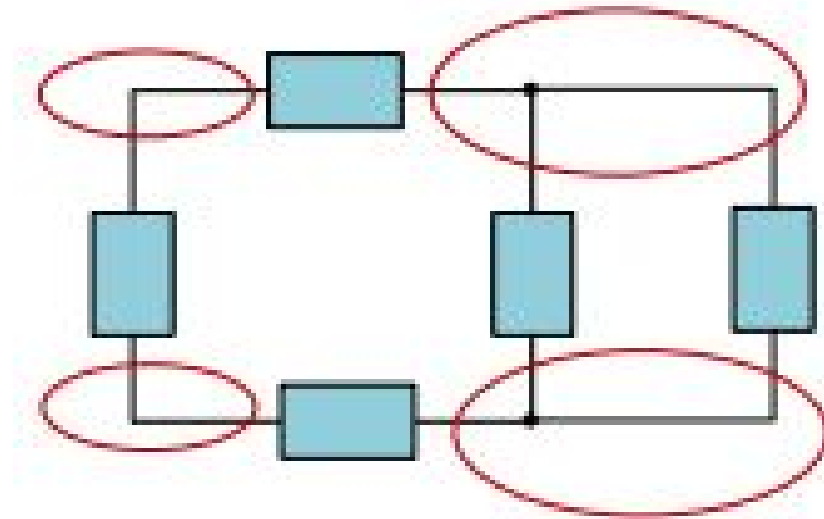
- Any place on a circuit where two or more circuit ELEMENTS meet.



Junction



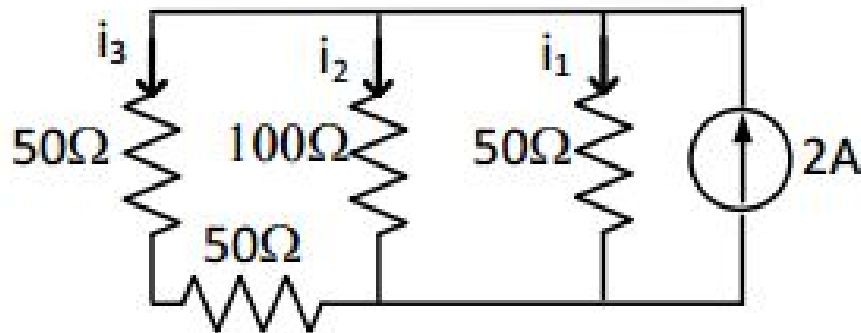- Any place on a circuit where two or more WIRES meet.




Kirchoff's Voltage Law (KVL)



Sum of the voltages around any loop = zero

$$\sum V_{\text{loop}} = 0$$

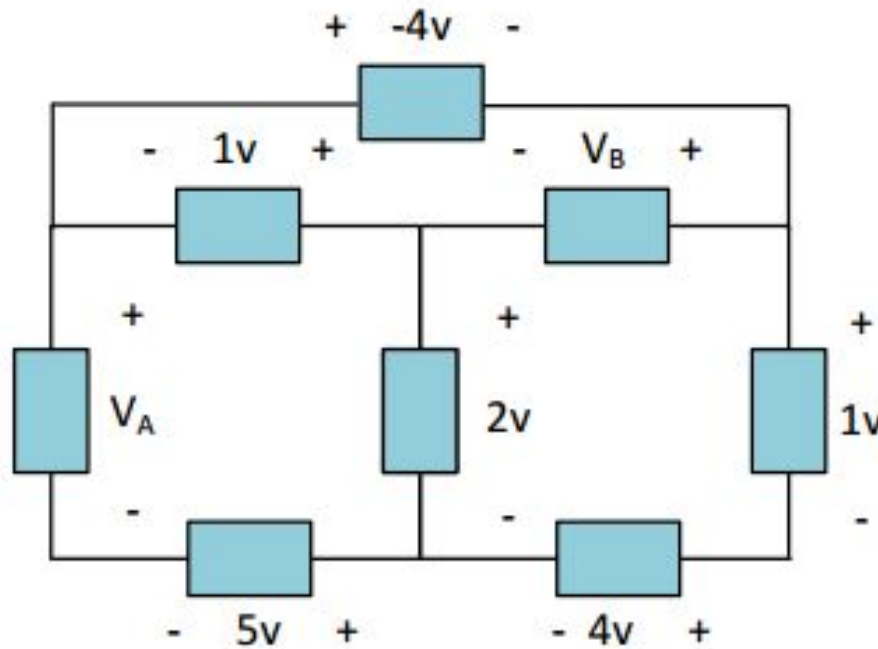


Kirchoff's Current Law (KCL)




Sum of the currents leaving a node =
sum of current entering the node

$$\sum i_{\text{leaving}} = \sum i_{\text{entering}}$$

(1)

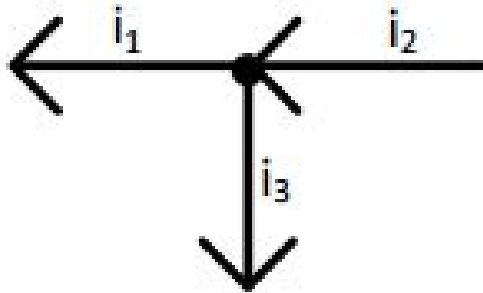

(2)

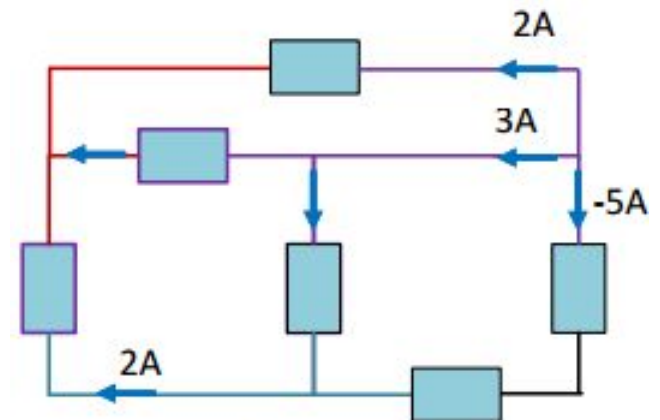


$$\sum i_{\text{leaving}} = 0$$

$$\sum i_{\text{entering}} = 0$$

$$\sum i_{\text{leaving}} = \sum i_{\text{entering}}$$



Breadboard

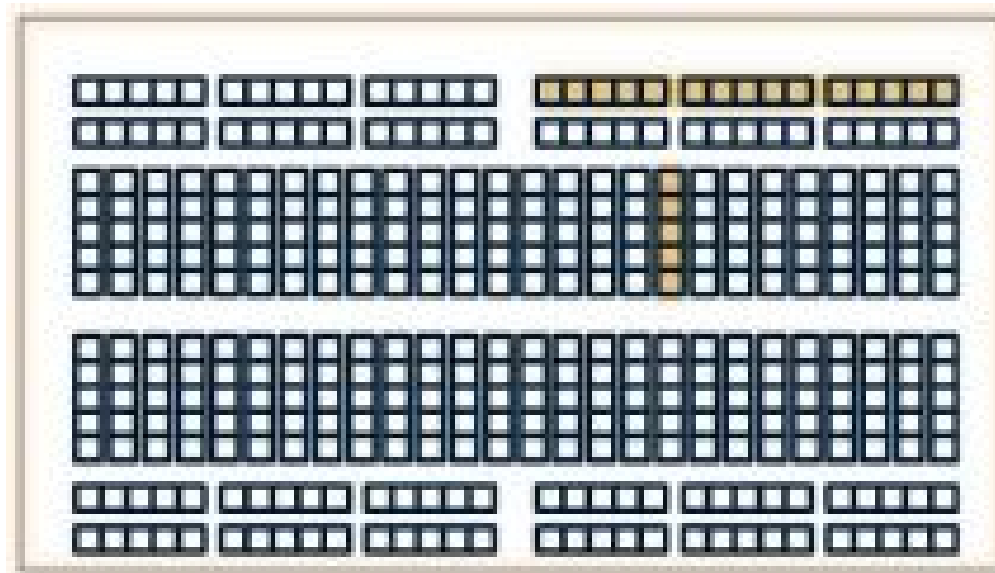

Circuit - Measure Current



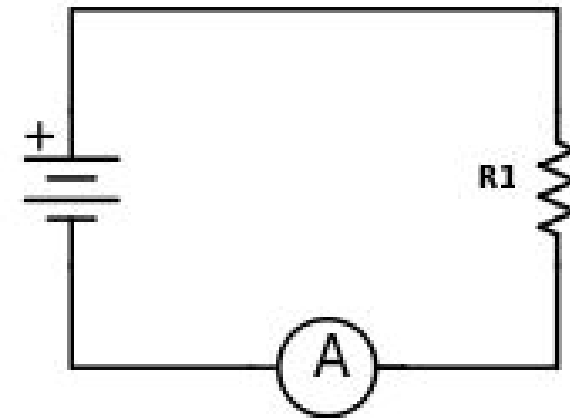
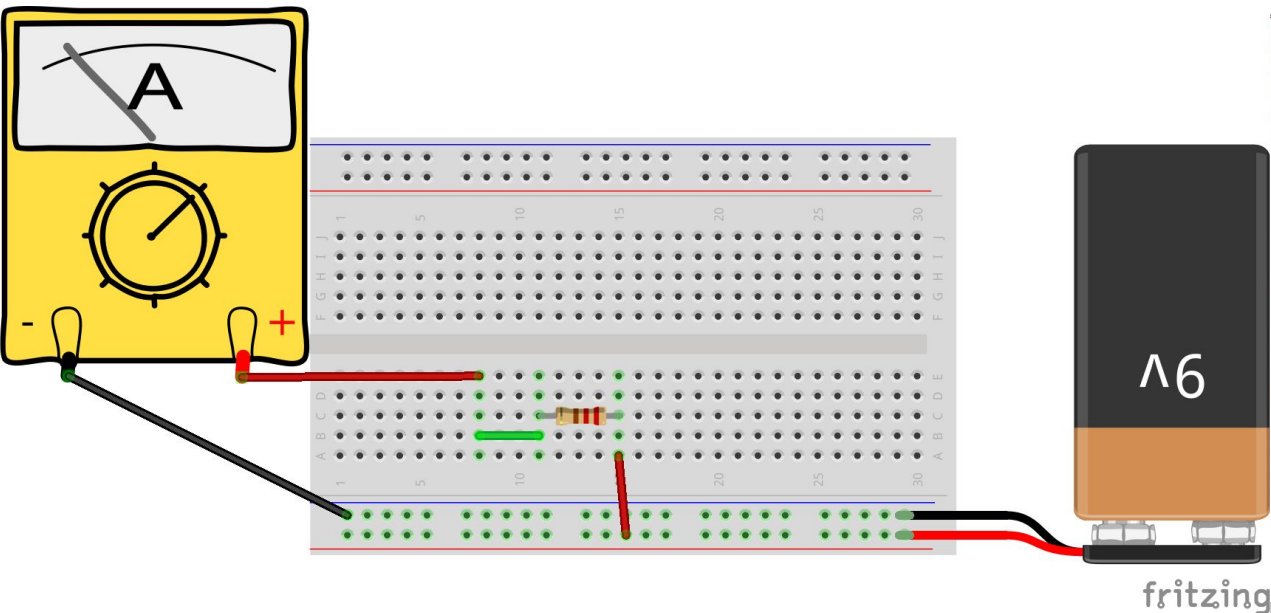
Ammeter connected in *series* with circuit



Circuit - Measure Voltage



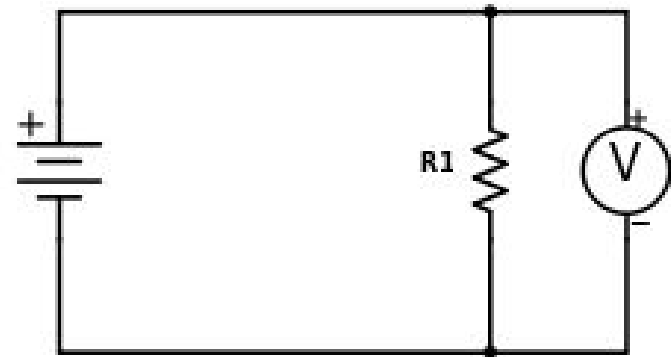
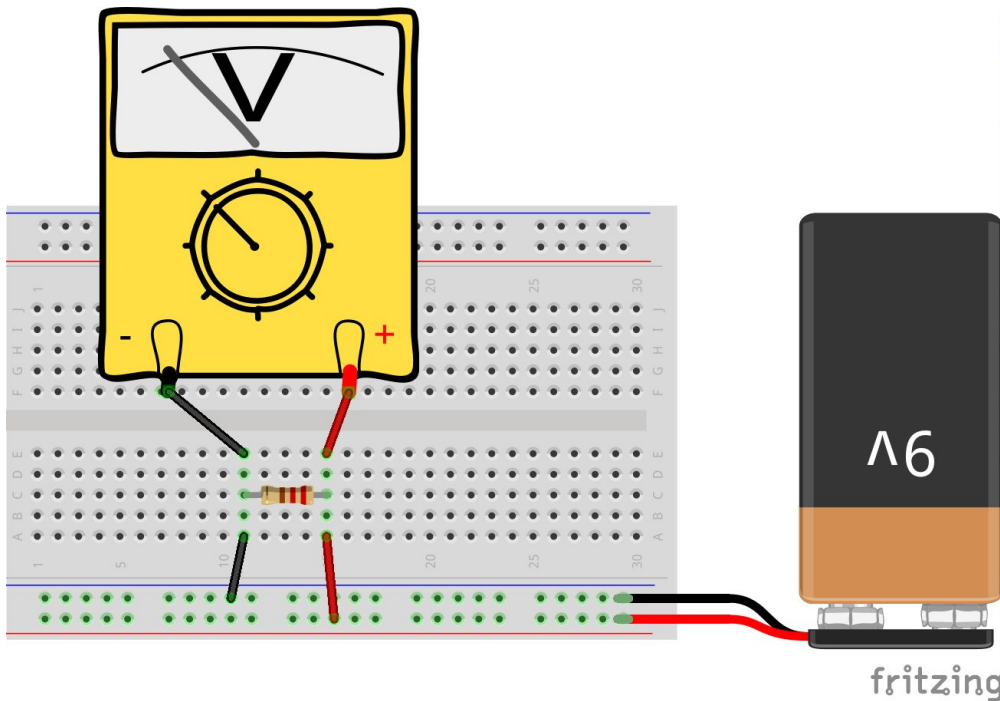
Voltmeter connected in *parallel* with circuit



Voltage Divider



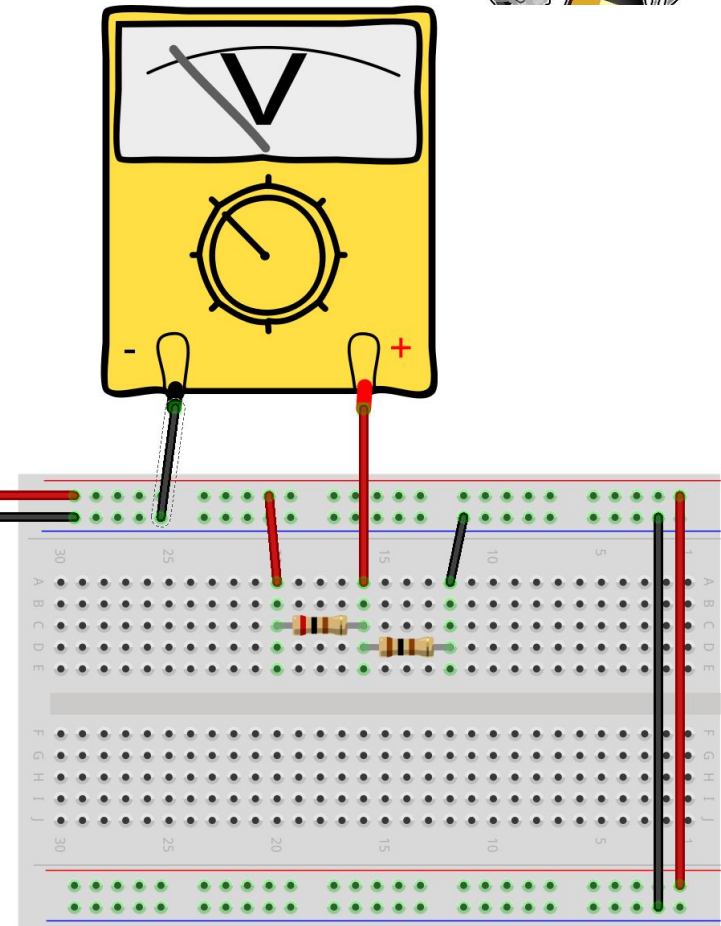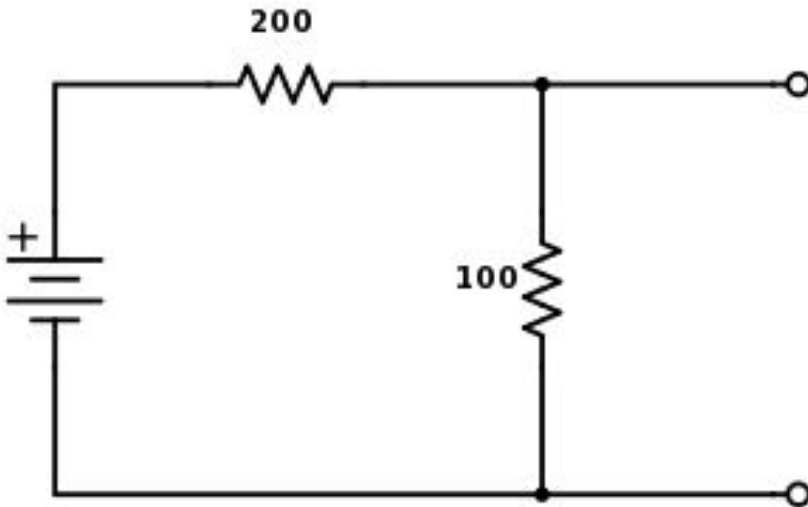
$$V_{out} = \frac{R_2}{(R_1 + R_2)} V_{in}$$




fritzing

RC Circuit

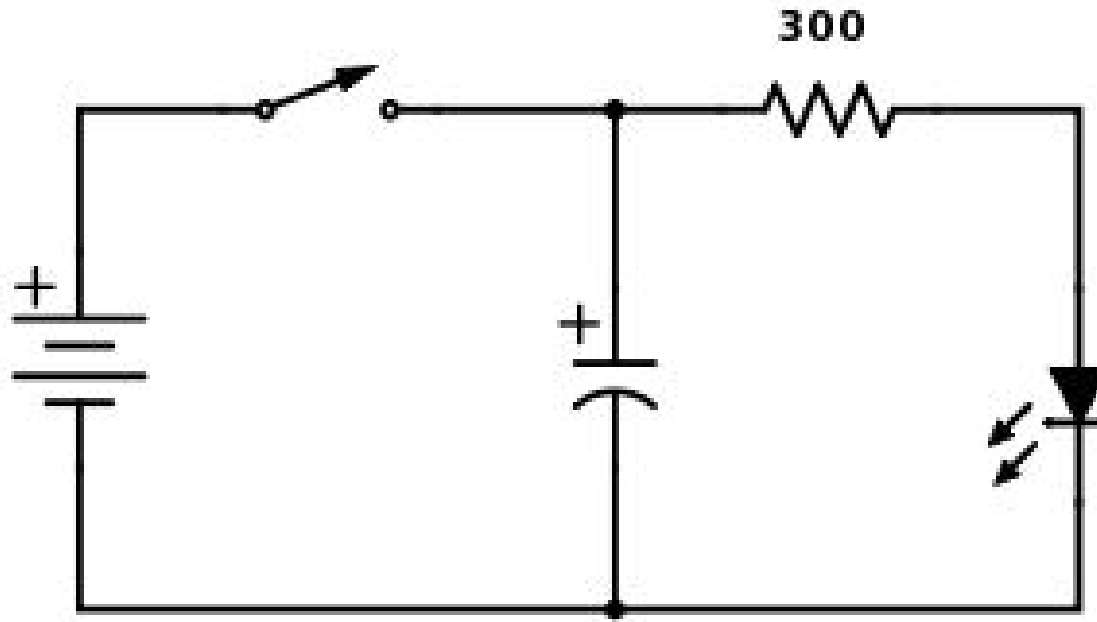

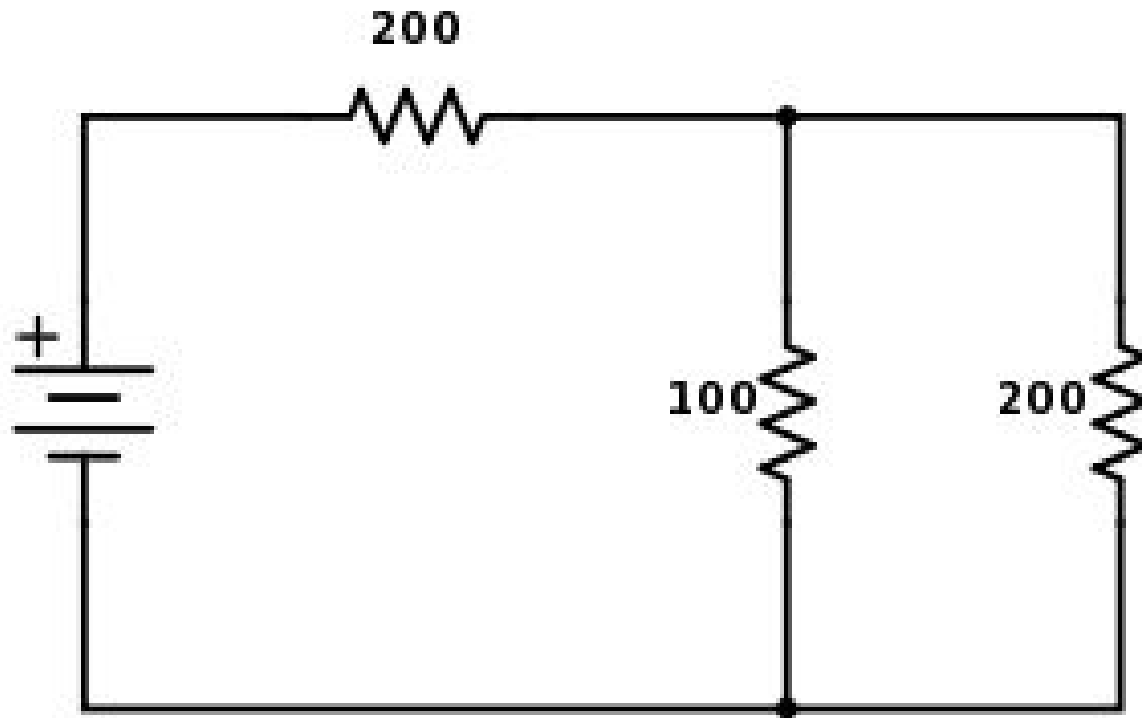Build Circuit and Measure Current Through R_{eq}




Challenge: Find R_{eq} of resistor cube



Assume all resistors are 100 ohm.

What if all resistors are 220 ohm?

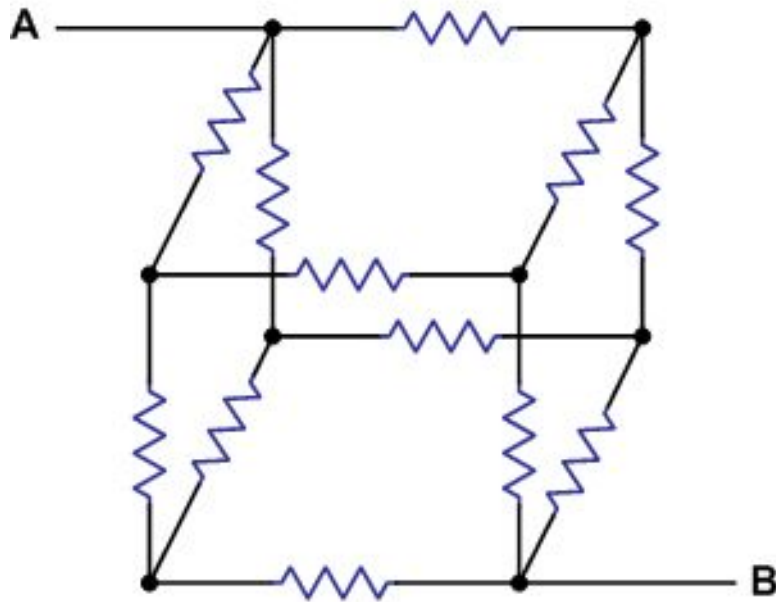



END