

Electrical Training

Week 1: Electricity, Voltage, Current, Resistance, Power, Breadboards, Github

Agenda



- Electrical subteams in RoboJackets
- Electricity basics
- Ohm's Law
- Breadboards
- Multimeters
- Github

RoboJackets Electrical




All teams require:

- basic electrical knowledge
- basic soldering
- wire crimping
- testing with multimeter






BattleBots

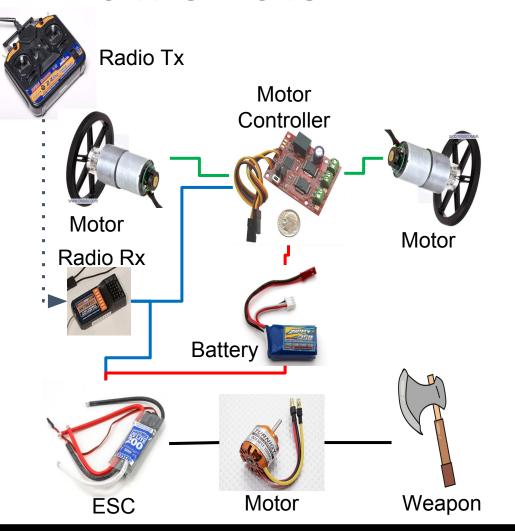



- Motor Operation
- Wireless control
- Power and durability
- Low focus on precision

FIRST Outreach

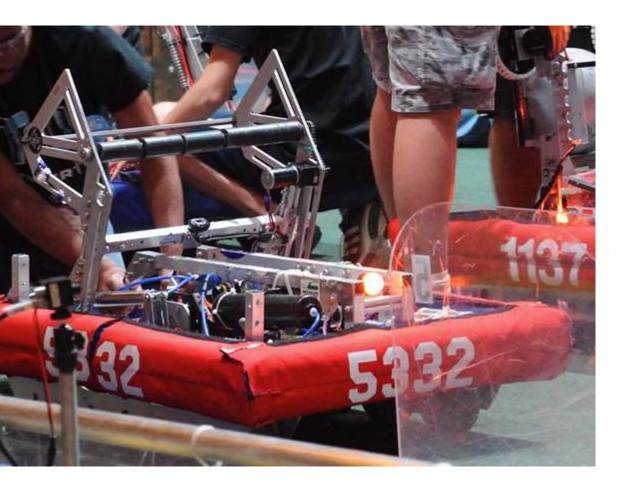




- Standard electrical parts
- Less emphasis on durability
- more emphasis on precision


RoboCup



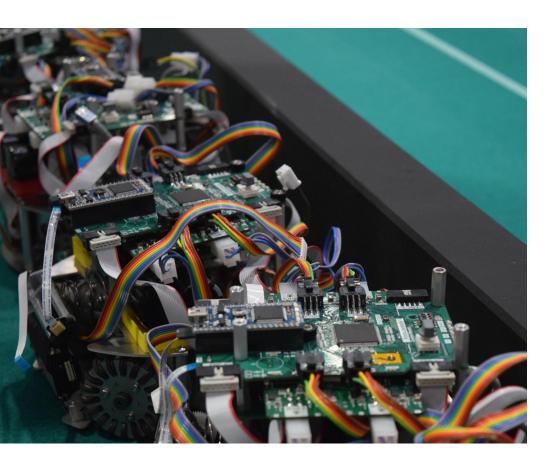

- Main focus on design
- Low focus on high power
- Extreme precision and accuracy
- All electrical boards custom-designed


IGVC

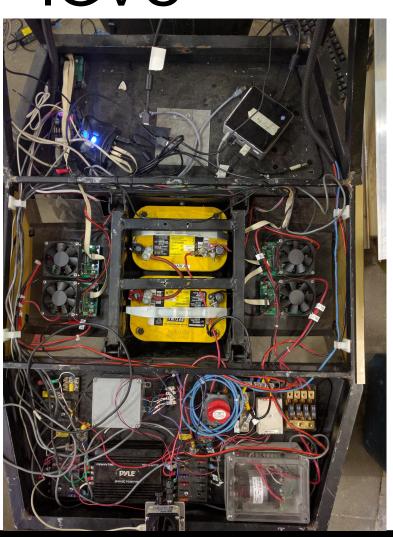

- Combination of custom and off-the-shelf components
- Multitude of sensors
- High-power motor operation
- Focus on maintaining and testing complex system

RoboRacing



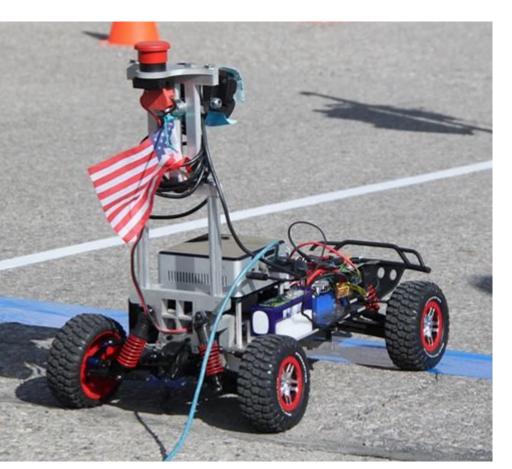

- Medium-power motor control
- System stability and durability
- Interface software and hardware with standard development board


What is electricity?




- The flow of electrons through a conductor
- We can describe this flow using:
 - voltage (V)
 - current (/)
 - resistance (R)
- Relate the 3 together by using Ohm's law:

$$V = I * R$$


Voltage (V)

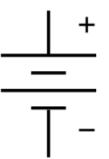

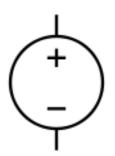



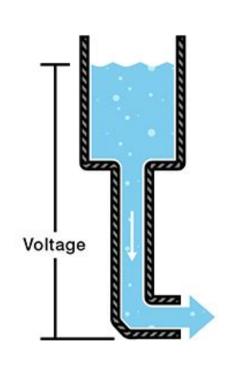
- The difference in potentials between 2 different locations
- The "pressure" with which electrons are thrust through a conductor
- water pipe analogy: the voltage resembles the downward pressure caused by water in a cylinder



Current (A)



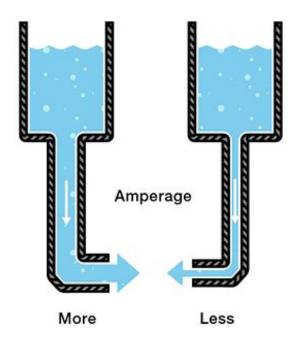The amount of charge flowing through a point in a conductor



Voltage and Current

voltage



current









"Voltage shocks, current kills"

Resistance (Ω)

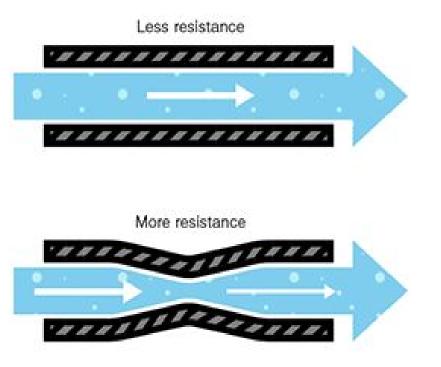- OBJ
- Used to control the amount of flow (current)
- Resistors provide this functionality



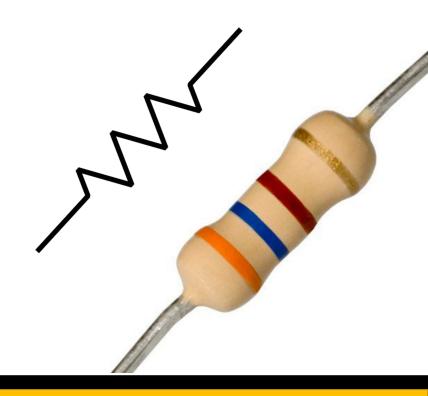

Ohm's Law



- V = I * R
- We can use resistance to control the flow of current at a point
- Similar to squeezing a water hose
 - press down -> water goes farther (with more pressure) but less goes through

Power



- Electrical components convert electricity to other forms of energy
 - Heat
 - Light
 - Motion
 - RF (...)
- Power expended by a component is:

$$P = V * I = I^2 * R = V^2 / R$$

 Components provide specification for how much power they can safely handle

Short and Open Circuits



Open Circuit - no connection between leads; *zero current*

No energy is expanded between leads

Short circuit - direct connection between leads; *zero voltage*

No voltage drop across leads

Short circuit across battery


Short:
$$R = 0$$
, $V = 9V$

$$I = V / R$$

$$I = 9V / 0 \rightarrow \infty$$

$$P \rightarrow \infty$$

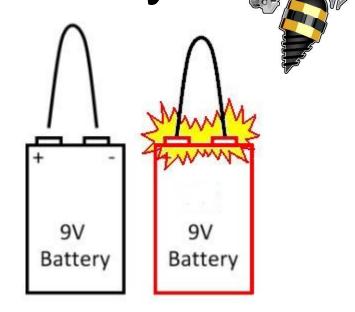Because all wire carries a small amount of resistance, a finite, albeit large, amount of power is expanded



- wires burn
- batteries explode
- robots cry


Measuring V, I, R

We use a multimeter.




Tools:


voltmeter

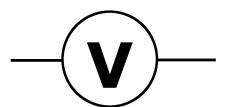

ammeter

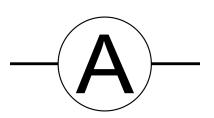


ohmmeter

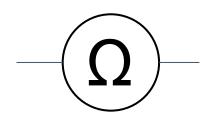


Measurements in a Circuit



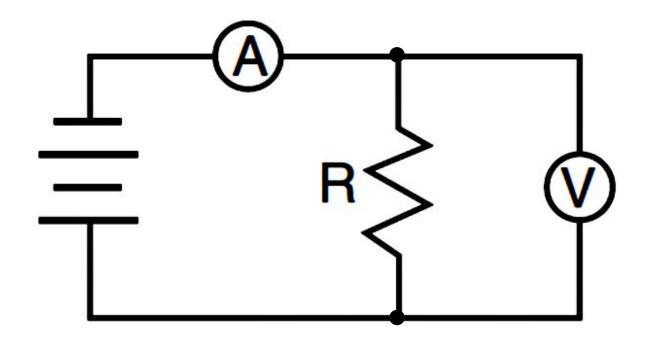

Breadboards allow us to easily create and test circuits

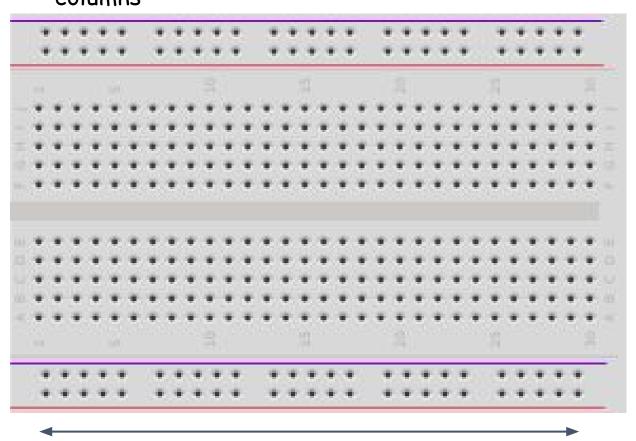
points are connected in voltage and ground columns




points are connected in a row

Circuit - Single Resistor



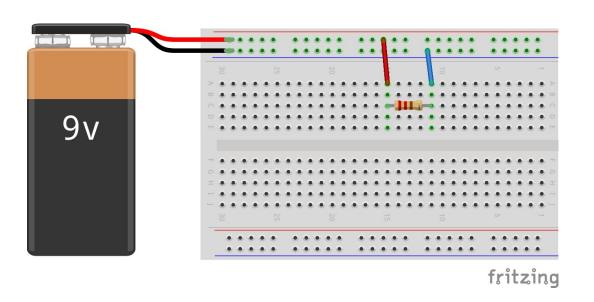


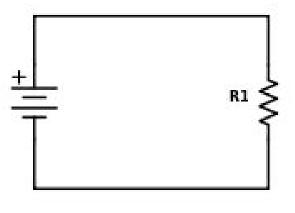


Circuit - Measure Current



Ammeter connected in series with circuit

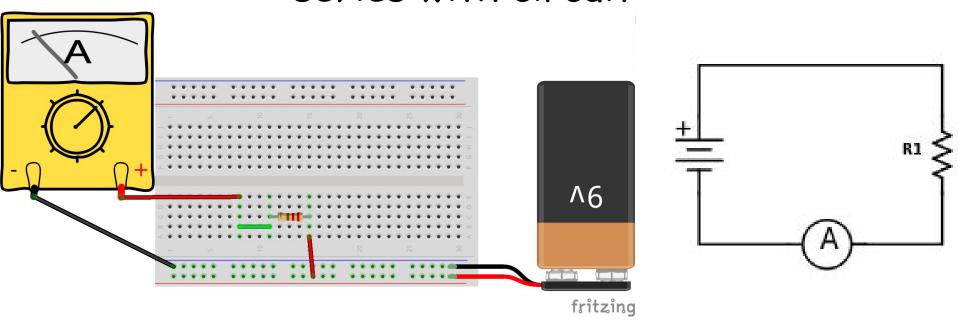

Circuit - Measure Voltage

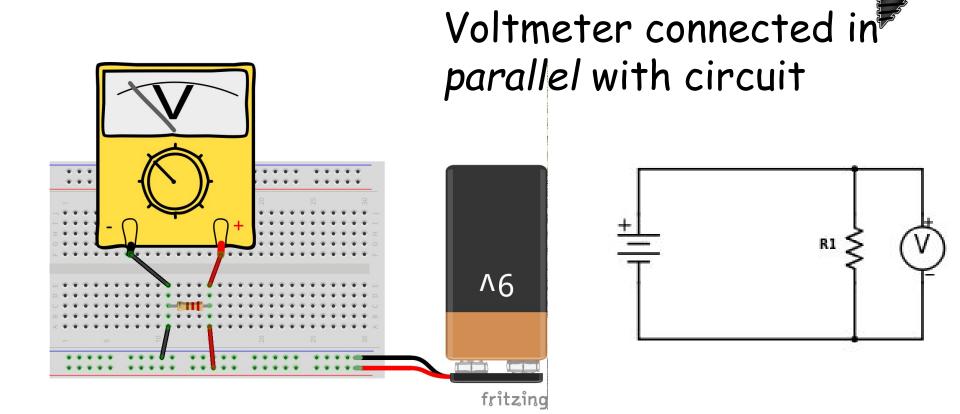





- Version control software
- Electrical Training content (presentations, schematics, code, etc.) can be found at:

github.com/RoboJackets/electrical-training